 


More Complex Gates

$$F = \overline{AB + CD} \Rightarrow N_{\text{tree}} \text{ will provide 0's, } P_{\text{tree}} \text{ will provide 1's}$$

$$\text{0's of function } F \text{ is } \overline{F}, \Rightarrow \overline{F} = \overline{\overline{AB + CD}} = AB + CD$$

*n*MOS transistors need high true inputs, so it is desirable for all input variables to be high true, just as above.




Likewise, a P_{tree} will provide 1's.

$$F = \overline{AB + CD}, \quad \text{need a form involving } \overline{A}, \overline{B}, \overline{C}, \overline{D}$$

Apply DeMorgan's Theorem:

$$F = \overline{AB} \cdot \overline{CD} = (\overline{A} + \overline{B}) \cdot (\overline{C} + \overline{D})$$

Implementation \Rightarrow

 

Can also use K-maps:

$$F = \overline{AB} + CD$$

	AB			
	1	1	0	1
1	1	1	0	1
0	0	0	0	0
1	1	1	0	1

For N_{tree} , minimize 0's; for P_{tree} , minimize 1's


	AB			
		0		
		0		
0	0	0	0	
		0		

$$N_{tree} = AB + CD$$

	AB			
	1	1		1
	1	1		1
	1	1		1

$$\begin{aligned}
 P_{tree} &= \overline{A} \cdot \overline{C} + \overline{A} \cdot \overline{D} + \overline{B} \cdot \overline{C} + \overline{B} \cdot \overline{D} \\
 &= \overline{A} (\overline{C} + \overline{D}) + \overline{B} (\overline{C} + \overline{D}) \\
 &= (\overline{A} + \overline{B}) \cdot (\overline{C} + \overline{D})
 \end{aligned}$$


Tri State Inverter

 

EN	I	O
0	X	Z
1	0	1
1	1	0


"Z" is high impedance state

Implementation? Here is one method:

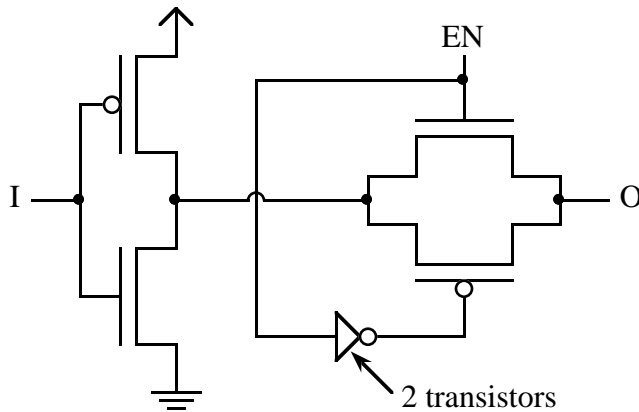


6 transistors total

Alternate representations:

 


or

 

where the connection for \overline{EN} is understood or implied, \overline{EN} still needs to somehow be provided in the physical circuit

Transmission Pass Gate Logic

 


Will require

$$(4 \text{ transistors for two pass gates}) + (2 \text{ transistors for inversion of } S) = 6 \text{ transistors total}$$

This technique uses less transistors than a design using normal gates, but is non-restoring. Pass gate logic has no drive capability. Drive comes from original A, B inputs.


A D-Latch using transmission gates:

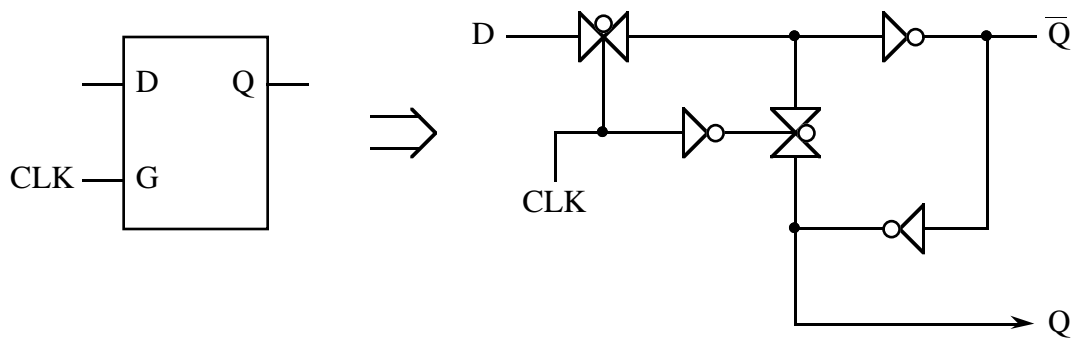


when $CLK = 1,$ $Q = D$
 $CLK = 0,$ $Q = Q_{old}$

Recall flip-flop construction from CAD course (edge triggered device) —
 → two latches in a master-slave arrangement are required


Falling edge triggered

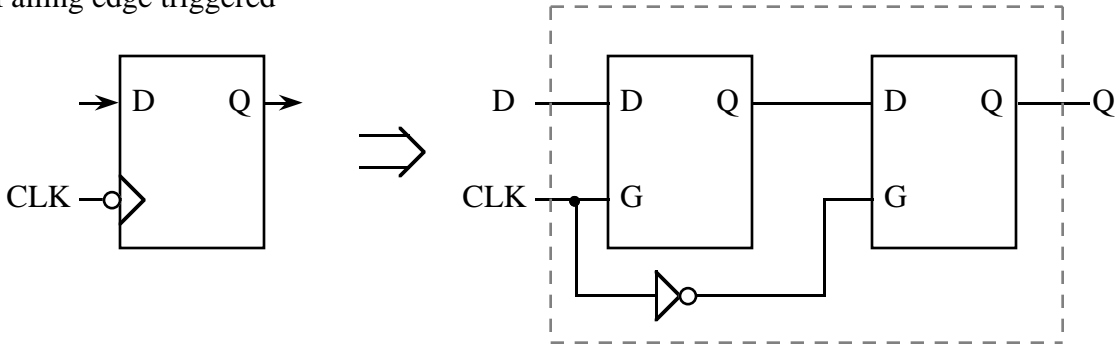

Rising edge triggered

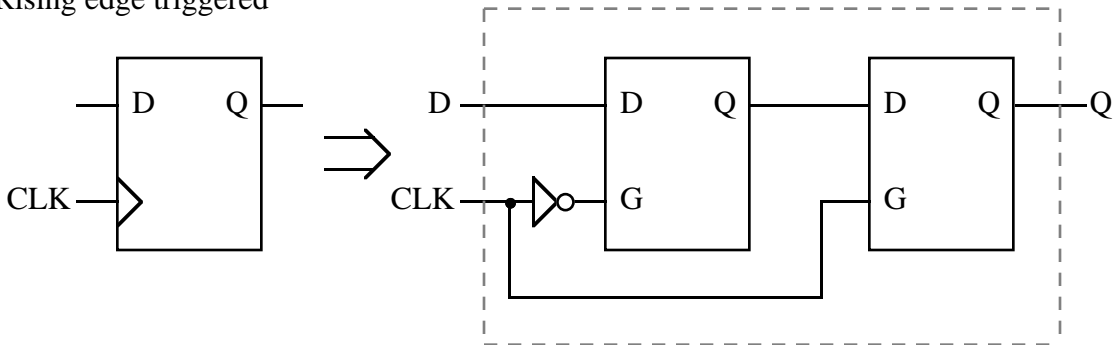

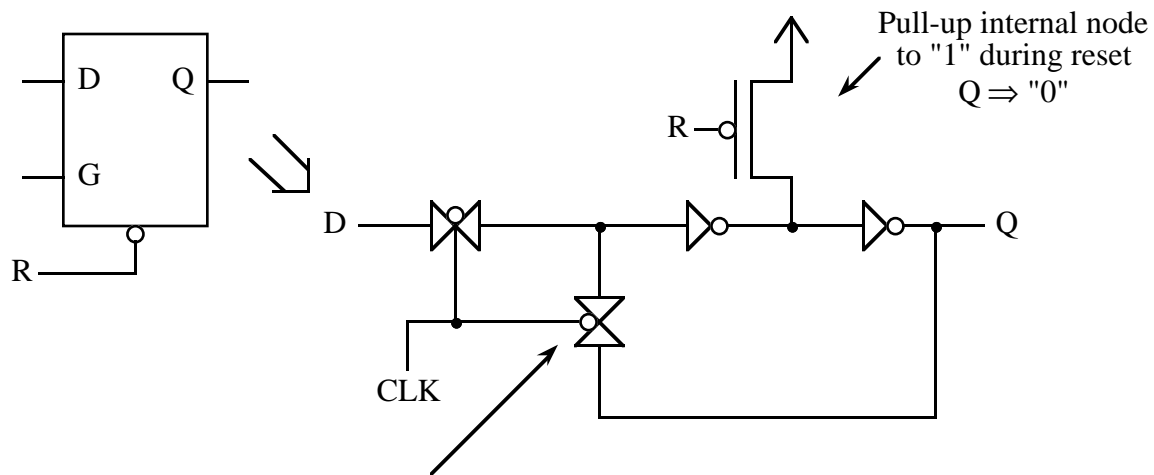
How would a D-Latch with an asynchronous reset be implemented?



Note: when connected to inverted terminal of transmission gate, then the inverter is implied

Introduction to Static Load Inverters

1)

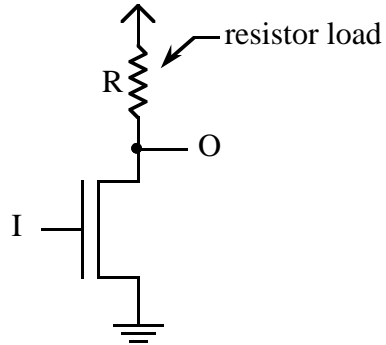

When $I = 1$, inverter dissipates static power.


Switching point of inverter depends on ratio of R to R_{ON} (on resistance of n MOS device).

$$V_{OH} = 5V,$$

$$V_{OL} \approx 0V, \text{ depends on ratio of } R/R_{On}$$

Note: output can swing from 0V to 5V (V_{dd})

2)

 

Load is enhancement-mode n MOS device.

Again, static power dissipation occurs when $I = 1$.


Note: output swings from $\approx 0V$ to $(V_{dd} - V_{Tn})$

Using a transistor as a load tends to require much less silicon area than a resistor.

$$V_{OH} = V_{dd} - V_{Tn},$$


$$V_{OL} \approx 0V, \text{ depending on ratio of } R_{ON} \text{ of two enhancement devices}$$

Depletion-mode *n*MOS

 

*n*MOS device with $V_{Tn} < 0V$ (negative threshold voltage). Device is always conducting if $V_{GS} > 0V$.

3)

 

$V_{GS} = 0V$ always


Load device is always on, looks like a load resistor.

Dissipates static power when $I = 1$

$V_{OH} = 5V$; $V_{OL} \approx 0V$, depending on ratio of $R_{ON,dep}$ to $R_{ON,enh}$.

Depletion-mode devices were used before it was economical to put both *p*-type and *n*-type devices on the same die.

4) *p*MOS device as static load

 


Here also the load device is always on (conducting).

Dissipates static power when $I = 1$.

$V_{OH} = 5V$; $V_{OL} \approx 0V$, depending on ratio of $R_{ON,p}$ to $R_{ON,n}$

Basic MOS Device Equations

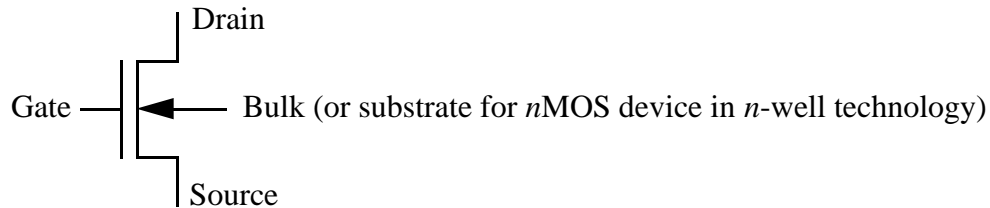

The n MOS device is a *four* terminal device: Gate, Drain, Source, Bulk.

Bulk (substrate) terminal is normally ignored at schematic level, usually tied to ground for the n MOS case. In analog applications, however, the bulk terminal may not be ignored.

Gate controls channel formation for conduction between Drain and Source. Drain at higher potential than Source — Source usually tied to GND to act as pull-down (n MOS).

Three regions of operations — first-order (*ideal*) equations:

Cutoff region

$$I_D = 0A \quad V_{GS} \leq V_{Tn} \text{ (nMOS threshold voltage)}$$

Linear region

$$I_D = \beta \left((V_{GS} - V_{Tn}) V_{DS} - \frac{V_{DS}^2}{2} \right) \quad 0 < V_{DS} < V_{GS} - V_{Tn}$$

Note: I_D is linear with respect to $(V_{GS} - V_{Tn})$ only when $\frac{V_{DS}^2}{2}$ is small.

Saturation region

$$I_D = \frac{\beta}{2} (V_{GS} - V_{Tn})^2 \quad 0 < V_{GS} - V_{Tn} < V_{DS}$$

Device parameters:

β = transistor gain factor, dependent on process parameters and device geometry

$$\beta = \left(\frac{\mu \epsilon}{t_{ox}} \right) \left(\frac{W}{L} \right)$$

↙ process dependent, constant
 ↘ under control of the designer

As W/L increases, effective R_{ON} of device decreases

μ = surface mobility of the carriers in the channel

ϵ = permittivity of the gate insulator

t_{ox} = thickness of the gate insulator

See Figure 2.5, 2.8 concerning μ , ϵ , and t_{ox}



SPICE represents β by a factor given by

$$K' = \mu C_{ox} = \mu \frac{\epsilon}{t_{ox}} = \mathbf{KP}$$

So,

$$I_D = \frac{K'}{2} \frac{W}{L} (V_{GS} - V_{Tn})^2; \quad \text{saturation region}$$

VI characteristic

  

Things to note:

In the "linear" region, I_D becomes less and less linear with V_{GS} as V_{DS} becomes large. This is because the $\frac{V_{DS}^2}{2}$ term in the linear region grows large.


Higher V_{GS} values increase channel conductance allowing for higher values of I_D for a given V_{DS} .

Predicting I_D values with ideal equations

In saturation region,

$$I_D = K' \left(\frac{W}{L} \right) \frac{(V_{GS} - V_T)^2}{2}$$

If we have

 

then we can calculate I_D based on V_{in} , K' , V_T (MOSFET parameters).

In specifying W , L values, these are often given in a dimensionless unit called lambda.

When mapping the transistor schematic/layout to a particular technology, the actual W , L will be calculated as:

$$\begin{aligned} W' \text{ (actual, microns } (\mu)) &= W \times \text{lambda (microns)} \\ L' \text{ (actual, microns)} &= L \times \text{lambda (microns)} \end{aligned}$$

So lambda is a scaling factor. Note that the ratio $\frac{W}{L}$ is what is important, and that

$$\frac{W'}{L'} = \frac{W \times \text{lambda}}{L \times \text{lambda}} = \frac{W}{L} \cdot$$

Scaling factor lambda allows transistor $\frac{W}{L}$ values specified in schematics to be technology independent.

For MOSIS foundry vendors,


2.0 μ technology \Rightarrow lambda = 1.0

1.2 μ technology \Rightarrow lambda = 0.6

0.8 μ technology \Rightarrow lambda = 0.4.

Note, however, that lambda *is not* always $\frac{1}{2}$ technology minimum feature size (line width). Scaling factor lambda *is* foundry/silicon vendor dependent.


In schematic,

 

mapped to 1.2 μ technology,

$$\frac{W}{L} = \frac{10.8\mu}{1.2\mu}$$

nMOSFET layout:

 

In digital logic, typically will draw all transistors with the minimum gate length ($= 2 \times \lambda$) and vary the width.

Larger $W \Rightarrow$ larger transconductance (more current flow for given gate voltage), higher gate capacitance

During fabrication process, the actual width and length of the channel can be *reduced* by diffusion from the bulk, source, and drain into the device channel.

SPICE has some MOSFET model parameters to account for this effect, L_D and W_D , where the actual the actual length and width is calculated as

$$L_{\text{effective}} = L_{\text{drawn}} - 2 \times L_D$$

$$W_{\text{effective}} = W_{\text{drawn}} - 2 \times W_D$$

If L_D , W_D parameters not specified in the model, then SPICE assumes they are 0.