
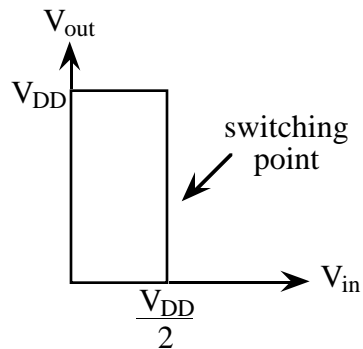


Ideal Inverter

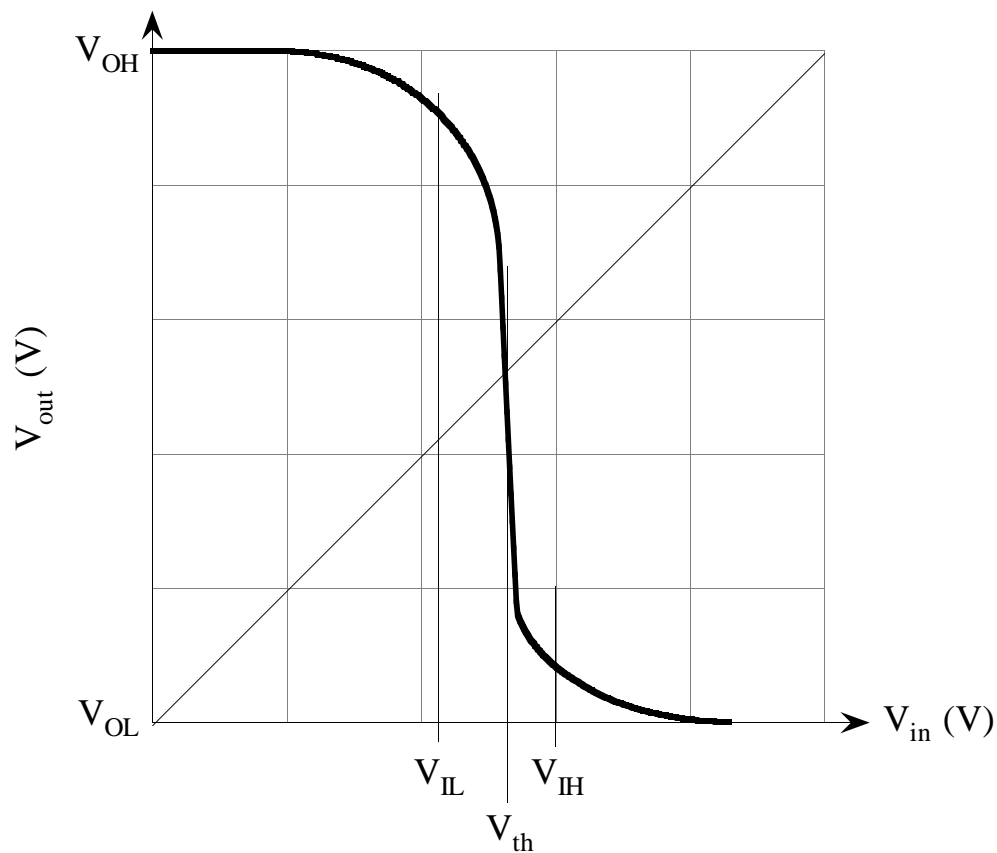


Actual Inverter Characteristics, some definitions



- V_{IL} represents the maximum logic 0 (LOW) input voltage that will guarantee a logic 1 (HIGH) at the output
- V_{IH} represents the minimum logic 1 (HIGH) input voltage that will guarantee a logic 0 (LOW) at the output

Noise Margin

Illustration of Noise Margin:

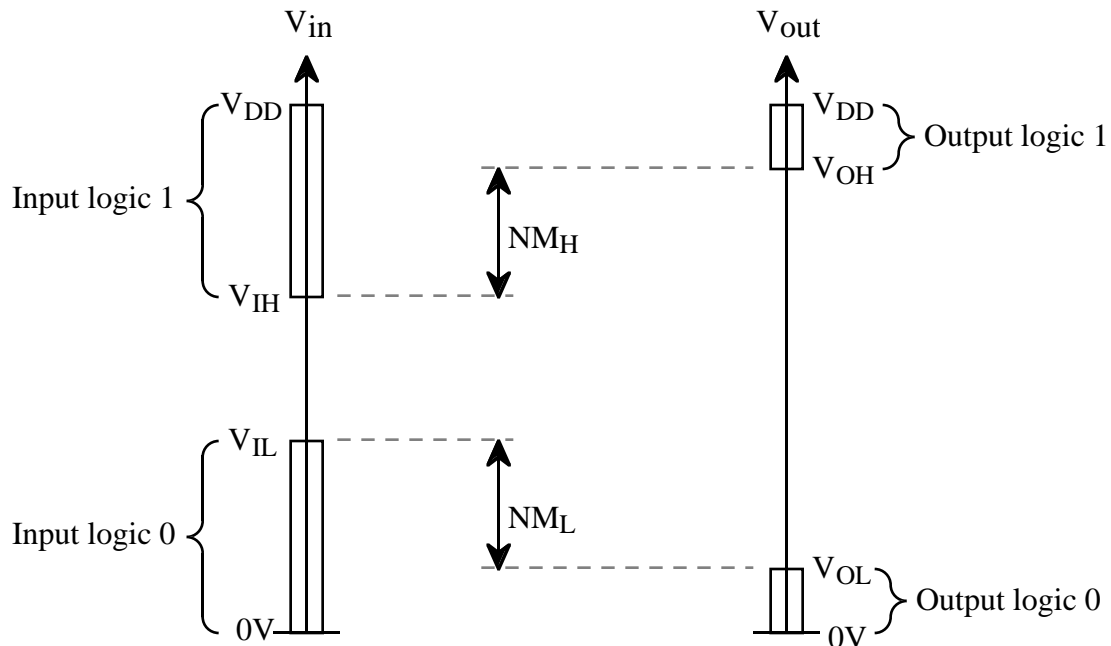

Calculate noise margin using


$$NM_L = V_{IL} - V_{OL}$$

$$NM_H = V_{OH} - V_{IH}$$

How do we determine V_{IL} , V_{OL} , V_{OH} , and V_{IH} ?

We must examine the inverter's transfer characteristic.

CMOS Inverter Regions of Operation

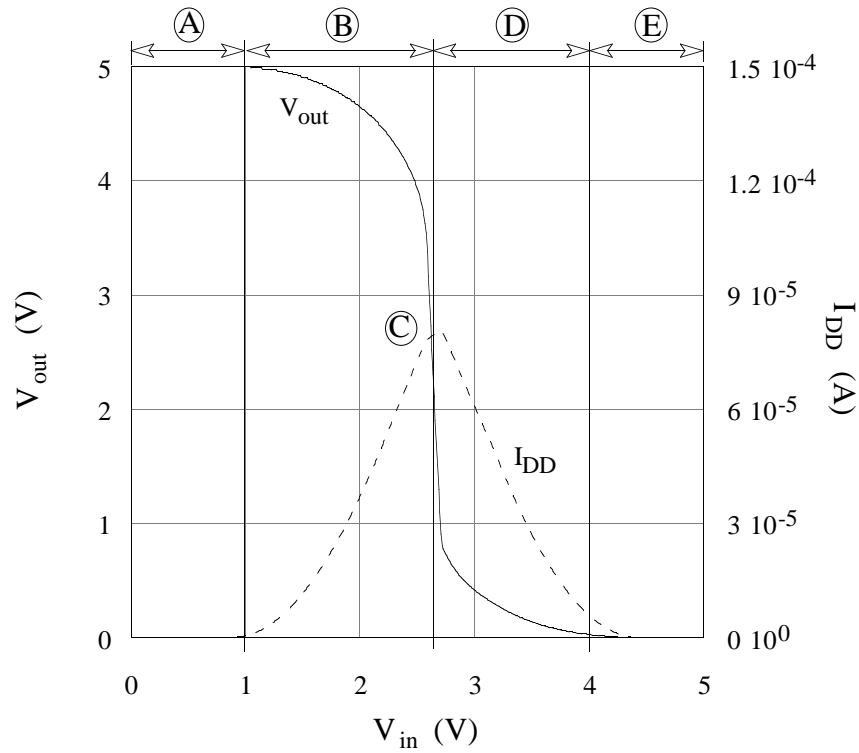

Region A:

$$0 \leq V_{in} < V_{Tn} \quad \Rightarrow \quad p\text{MOS nonsaturated (cutoff); } n\text{MOS cutoff}$$

- $n\text{MOS}$ is cutoff because $V_{in} < V_{Tn}$

Why is the $p\text{MOS}$ device in the linear region?

$$\text{Linear region} \equiv V_{SDp} < V_{SGp} - |V_{Tp}|$$

$$(5-5)\text{V} < (5-0)\text{V} - |-0.7|\text{V}$$

$$[\text{for } V_{DD} = 5\text{V and } V_{Tp} = -0.7\text{V}]$$

$$0\text{V} < 4.3\text{V}$$

Note that the $p\text{MOS}$ device can be in linear region even if $I_{Dp} \approx 0\text{A}$!

Region B:

$$V_{Tn} \leq V_{in} < V_{th} \quad \Rightarrow \quad p\text{MOS nonsaturated, } n\text{MOS saturated}$$

Why is $n\text{MOS}$ saturated? Is $V_{DSn} > V_{GSn} - V_{Tn}$?

Because $(V_{DSn} = V_{out}) > V_{th}$ and $(V_{GSn} = V_{in}) < V_{th}$,

$$\begin{aligned} \text{then} \quad & V_{DSn} > V_{GSn} - V_{Tn} \\ & V_{out} > V_{in} - V_{Tn} \end{aligned} \quad [\text{B-1}]$$

Why is $p\text{MOS}$ in linear region?

It started out in linear and will remain in linear as long as

$$\begin{aligned} V_{SDp} &< V_{SGp} - |V_{Tp}| \\ (V_{DD} - V_{out}) &< (V_{DD} - V_{in}) - |V_{Tp}| \\ V_{in} &< V_{out} - |V_{Tp}| \end{aligned} \quad [\text{B-2}]$$

V_{out} in the above expression (Eqn. [B-2]) is decreasing towards V_{th} and V_{in} is increasing towards V_{th} . When Eqn. [B-2] no longer holds, then the $p\text{MOS}$ device will become saturated.

For the $p\text{MOS}$ device, then

regions $A \Rightarrow B \Rightarrow C$ correspond to
linear \Rightarrow linear \Rightarrow saturated, respectively.

How can you predict the output voltage for region B?

The n MOS is saturated, so $I_{Dn} = \frac{\beta_n}{2} (V_{in} - V_{Tn})^2 = \frac{\beta_n}{2} (V_{GSn} - V_{Tn})^2$


The p MOS is linear, so

$$I_{Dp} = \frac{\beta_p}{2} (2(V_{SGp} - |V_{Tp}|)V_{SDp} - (V_{SDp})^2)$$


$$I_{Dp} = \frac{\beta_p}{2} (2(V_{DD} - V_{in} - |V_{Tp}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2)$$

Can solve for V_{out} since

$$I_{Dn} = I_{Dp}$$

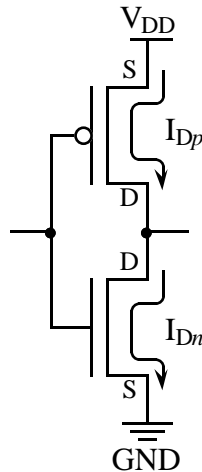

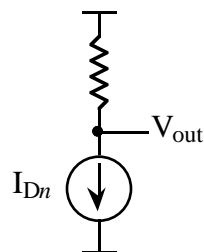Equivalent circuit for region B \Rightarrow



Region C:

$$V_{in} = V_{th} \quad \Rightarrow \quad p\text{MOS saturated, } n\text{MOS saturated}$$

In order for $n\text{MOS}$ to be saturated, need

$$V_{DSn} > V_{GSn} - V_{Tn}$$

$$V_{out} > V_{in} - V_{Tn}$$

In order for $p\text{MOS}$ to be saturated, need

$$V_{SDp} > V_{SGp} - |V_{Tp}|$$

$$V_{DD} - V_{out} > V_{DD} - V_{in} - |V_{Tp}|$$


$$V_{out} < V_{in} + |V_{Tp}|$$

So V_{out} in region C,

$$V_{in} - V_{Tn} < V_{out} < V_{in} + |V_{Tp}|$$

The CMOS inverter has very high gain in region C so small changes in V_{in} produce large changes in V_{out} . No closed form equation for V_{out} . Somewhere in this region, $V_{out} = V_{in}$, which is the switching point for this gate.

Equivalent circuit for region C:

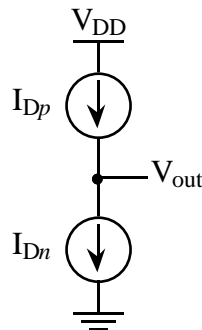

What is V_{in} in region C?

In region C, both devices in saturation so

$$I_{Dp} = \frac{\beta_p}{2} (V_{DD} - V_{in} - |V_{Tp}|)^2$$

$$I_{Dn} = \frac{\beta_n}{2} (V_{in} - V_{Tn})^2$$

So, using $I_{Dn} = I_{Dp}$, V_{in} can be solved for (more on this later....)

Region D:

$V_{th} < V_{in} \leq V_{DD} - |V_{Tp}| \Rightarrow p\text{MOS saturated, } n\text{MOS linear}$

Hence,
$$I_{Dp} = \frac{\beta_p}{2} (V_{DD} - V_{in} - |V_{Tp}|)^2$$

$$I_{Dn} = \frac{\beta_n}{2} (2(V_{in} - V_{Tn})V_{out} - V_{out}^2)$$

Again, since $I_{Dp} = I_{Dn}$, we can solve for V_{out} :

$$V_{out}^2 - 2(V_{in} - V_{Tn})V_{out} + \frac{\beta_p}{\beta_n} (V_{DD} - V_{in} - |V_{Tp}|)^2 = 0$$

using
$$x = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$


and, recognizing from above,

$$a = 1, b = -2(V_{in} - V_{Tn}), c = \frac{\beta_p}{\beta_n} (V_{DD} - V_{in} - |V_{Tp}|)^2$$

we get

$$V_{\text{out}} = (V_{\text{in}} - V_{\text{Tn}}) - \sqrt{(V_{\text{in}} - V_{\text{Tn}})^2 - \frac{\beta_p}{\beta_n} (V_{\text{in}} - V_{\text{DD}} - |V_{\text{Tp}}|)^2} .$$

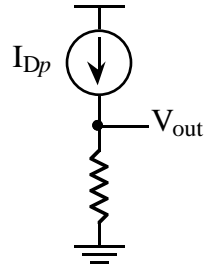Equivalent circuit for region D \Rightarrow



Region E:


$$V_{\text{in}} > V_{\text{DD}} - |V_{\text{Tp}}| \quad \Rightarrow \quad p\text{MOS is cutoff, } n\text{MOS is linear mode}$$

$$\text{Since } V_{\text{SGp}} = V_{\text{DD}} - V_{\text{in}} (< |V_{\text{Tp}}|),$$

$$\therefore V_{\text{out}} \approx 0\text{V}$$

due to $n\text{MOS}$ acting as pull-down while $p\text{MOS}$ in cutoff.

CMOS Inverter Transfer Characteristic

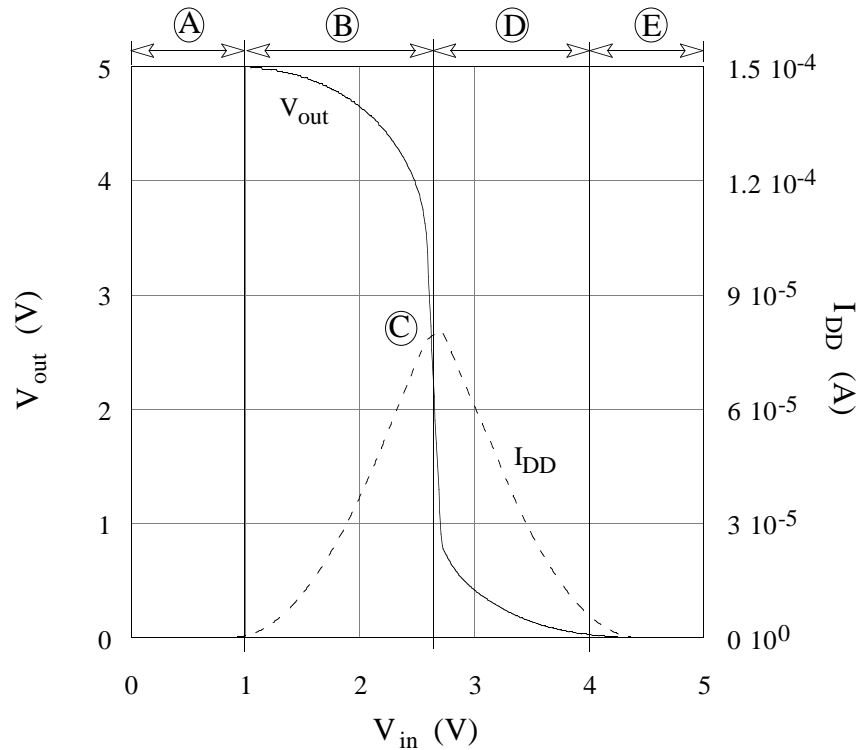

Analysis:

V_{OH} : $V_{in} < V_{Tn}$, the n MOS transistor is in cutoff while the p MOS transistor is turned-on (inversion layer established). The result is

$$V_{OH} \approx V_{DD}.$$

V_{OL} : $(V_{DD} - V_{in}) < |V_{Tp}|$, the p MOS is in cutoff while the n MOS is on and providing a conduction channel to ground. Hence,

$$V_{OL} \approx 0V.$$

V_{IL} : Input low voltage, here the n MOS transistor is saturated and the p MOS is nonsaturated. Equating the currents provides

$$\frac{\beta_n}{2} (V_{IL} - V_{Tn})^2 = \frac{\beta_p}{2} \left(2(V_{DD} - V_{IL} - |V_{Tp}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2 \right).$$

V_{IL}: (continued) Since two unknowns exist, $V_{in} = V_{IL}$ and V_{out} , a second equation is needed. Use the unity-gain condition to obtain this second equation,

$$\frac{dV_{out}}{dV_{in}} = \frac{(\partial I_{Dn}/\partial V_{in}) - (\partial I_{Dp}/\partial V_{in})}{(\partial I_{Dp}/\partial V_{out})} = -1,$$

provides

$$V_{IL} \left(1 + \frac{\beta_n}{\beta_p} \right) = 2V_{out} + \frac{\beta_n}{\beta_p} V_{Tn} - V_{DD} - |V_{Tp}|.$$

Now the two equations needed to solve for V_{IL} and V_{out} exist.

V_{IH}: Input high voltage, here the n MOS is nonsaturated and the p MOS is saturated. Equating the drain currents yields

$$\frac{\beta_n}{2} \left(2(V_{IH} - V_{Tn})V_{out} - V_{out}^2 \right) = \frac{\beta_p}{2} (V_{DD} - V_{IH} - |V_{Tp}|^2),$$

the first of two equations needed to solve two unknowns, $V_{in} = V_{IH}$ and V_{out} . Use the unity-gain condition to get the second,

$$\frac{dV_{out}}{dV_{in}} = \frac{(\partial I_{Dp}/\partial V_{in}) - (\partial I_{Dn}/\partial V_{in})}{(\partial I_{Dn}/\partial V_{out})} = -1.$$

This provides

$$V_{IH} \left(1 + \frac{\beta_p}{\beta_n} \right) = 2V_{out} + V_{Tn} + \frac{\beta_p}{\beta_n} (V_{DD} - |V_{Tp}|),$$

the second equation needed to solve for the two unknowns.

V_{th} : At the CMOS inverter's switching point, or *inverter threshold*, $V_{th} = V_{in} = V_{out}$ and both the p MOS and n MOS transistors are saturated. Again, equating the drain currents,

$$\frac{\beta_n}{2} (V_{th} - V_{Tn})^2 = \frac{\beta_p}{2} (V_{DD} - V_{th} - |V_{Tp}|)^2$$

is obtained which can be easily solved to provide V_{th} ,


$$V_{th} = \frac{V_{Tn} + \sqrt{\frac{\beta_p}{\beta_n} (V_{DD} - |V_{Tp}|)}}{\left(1 + \sqrt{\frac{\beta_p}{\beta_n}}\right)}.$$

Note: switching point of gate (V_{th}) is $\frac{V_{DD}}{2}$ -if- $\frac{\beta_n}{\beta_p} = 1$ and $V_{Tn} = -V_{Tp}$.

So, switching point of inverter is function of the ratio of the n MOS/ p MOS gains and the threshold voltages of the n MOS, p MOS transistors.

β_n / β_p Ratio

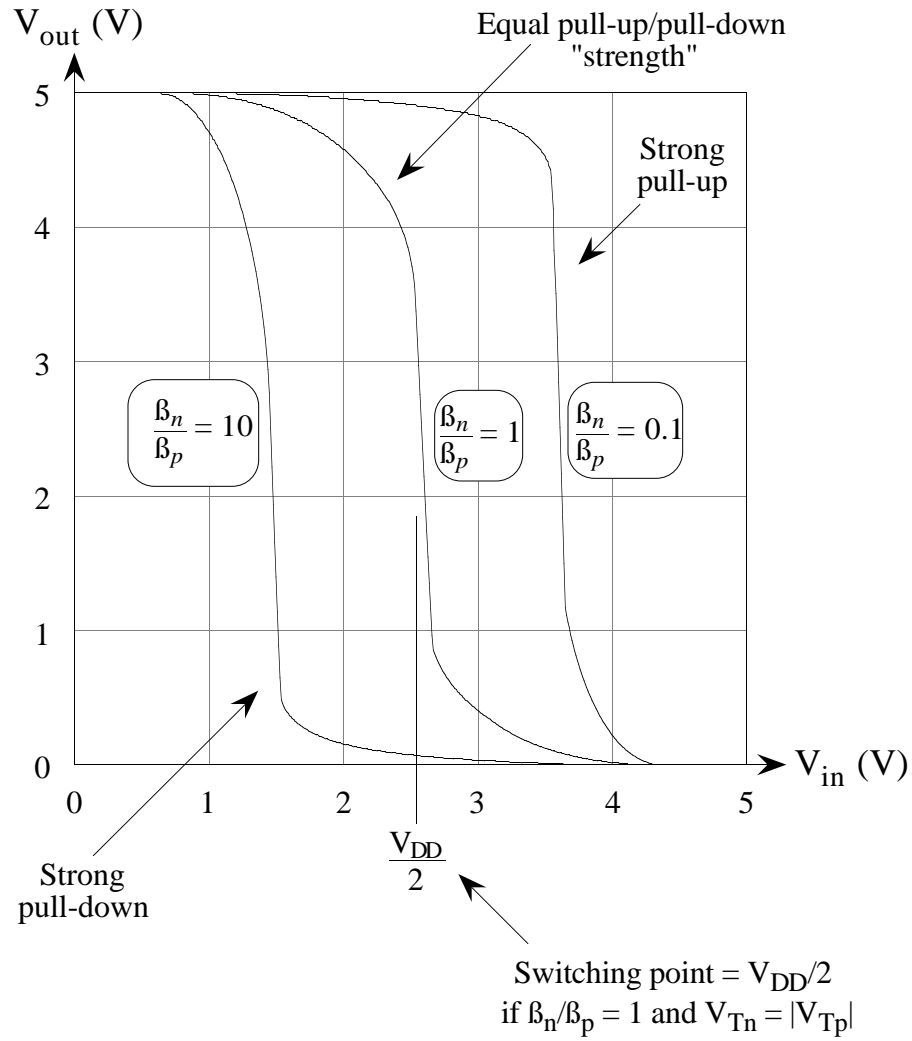The β_n (gain of n MOS) / β_p (gain of p MOS) ratio determines the switching point of the CMOS inverter.



Recall that

$$\beta = \frac{\mu \epsilon W}{t_{ox} L} .$$

If we assume that the n MOS and p MOS transistors have equal W/L ratios, then


$$\frac{\beta_n}{\beta_p} = \frac{\frac{\mu_n \epsilon \frac{W_n}{L_n}}{t_{ox}}}{\frac{\mu_p \epsilon \frac{W_p}{L_p}}{t_{ox}}} = \frac{\mu_n}{\mu_p} = \frac{\text{electron mobility}}{\text{hole mobility}} .$$

In silicon, the ratio μ_n/μ_p is usually between 2 to 3.

This means, that if $L_n = L_p$,


then W_p must be 2 to 3 times W_n

in order for $\beta_n = \beta_p$.

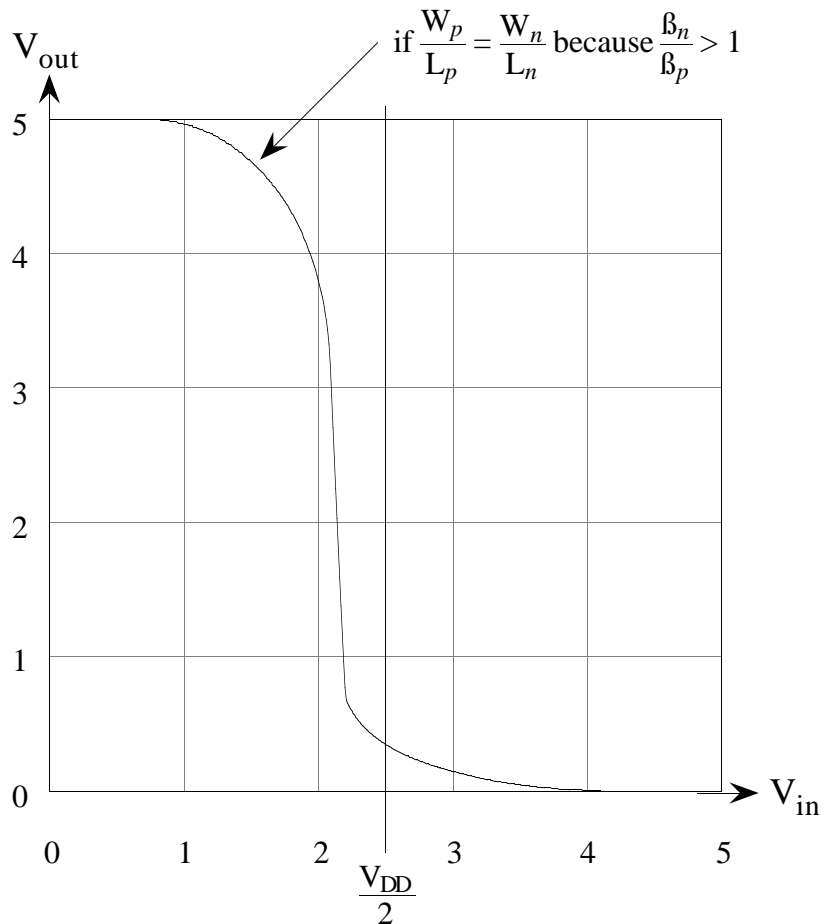

Calculate the switching point of a static load inverter as function of β_n/β_p :

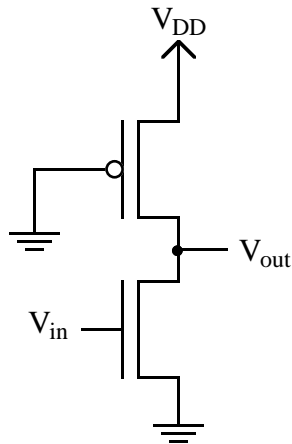In region C, already know n MOS device is saturated from previous analysis.



For p MOS to be saturated need:

$$V_{SDp} > V_{SGp} - |V_{Tp}|$$

$$V_{DD} - V_{out} > V_{DD} - 0V - |V_{Tp}|$$

$$V_{out} < |V_{Tp}|$$

Not true!!!

(If V_{out} in region C is about $\frac{V_{DD}}{2}$)

$$\text{and } \frac{V_{DD}}{2} > |V_{Tp}|$$

(typically this is true))

$\therefore p$ MOS must be in linear region

Then
$$I_{Dn} = \frac{\beta_n}{2} (V_{GSn} - V_{Tn})^2 = \frac{\beta_n}{2} (V_{in} - V_{Tn})^2$$

and
$$I_{Dp} = \frac{\beta_p}{2} (2(V_{SGp} - |V_{Tp}|)V_{SDp} - V_{SDp}^2)$$

$$I_{Dp} = \frac{\beta_p}{2} (2(V_{DD} - |V_{Tp}|)(V_{DD} - V_{out}) - (V_{DD} - V_{out})^2)$$

Equate $I_{Dn} = I_{Dp}$ and solve for V_{out} .

$$V_{out} = |V_{Tp}| + \sqrt{(V_{DD} - |V_{Tp}|)^2 - \frac{\beta_n}{\beta_p} (V_{in} - V_{Tn})^2}$$

Can also solve for β_n/β_p ,

$$\frac{\beta_n}{\beta_p} = \frac{(V_{DD} - |V_{Tp}|)^2 - (V_{out} - |V_{Tp}|)^2}{(V_{in} - V_{Tn})^2}$$

Consider again

$$\frac{\beta_n}{\beta_p} = \frac{(V_{DD} - |V_{Tp}|)^2 - (V_{out} - |V_{Tp}|)^2}{(V_{in} - V_{Tn})^2}$$

for the pseudo- n MOS inverter.

Let $|V_{Tp}| = V_{Tn} = 0.2V_{DD}$ and $V_{in} = V_{out} = \frac{V_{DD}}{2}$. Then, for $V_{DD} = 5V$,

$$\frac{\beta_n}{\beta_p} \approx 6.1 !!!$$

Note that this is *very* different result from the CMOS inverter case!

If $V_{DD} = 3.3V$, but the value of $V_{Tn} = |V_{Tp}|$ is unchanged (i.e., 1V in the above example), then

$$\frac{\beta_n}{\beta_p} \approx 11.5$$

for a switching point equal to $\frac{V_{DD}}{2}$.

The β_n/β_p ratio depends on the absolute value of V_{DD} ! This means that the operation of the pseudo- n MOS inverter will NOT scale with V_{DD} (for a given CMOS technology).

For the CMOS inverter, the β_n/β_p ratio for a switching point of $V_{DD}/2$ is *independent* of V_{DD} so its operation will scale with supply voltage. This is a another big advantage of CMOS technology.

Not unusual for static CMOS circuits to operate over a very large range of power supply voltages, i.e., 2.0V to 6.0V is common.